

Bit Slicing

Repetitive Logic

Where logic blocks are duplicated within a system, there is much to gain from optimization.

- Optimize single block for size.

The effect is amplified by the number of identical blocks.


- Optimize interconnect.

With careful design, the requirement for routing channels between the blocks can be eliminated.

Interconnection is by butting in 2 dimensions.


Bit Slicing

 Instead of creating an ALU function by function, we create it slice by slice.





- Each *bit slice* is a full 1-bit ALU.
- N are used to create an N -bit ALU.

Bit Slicing

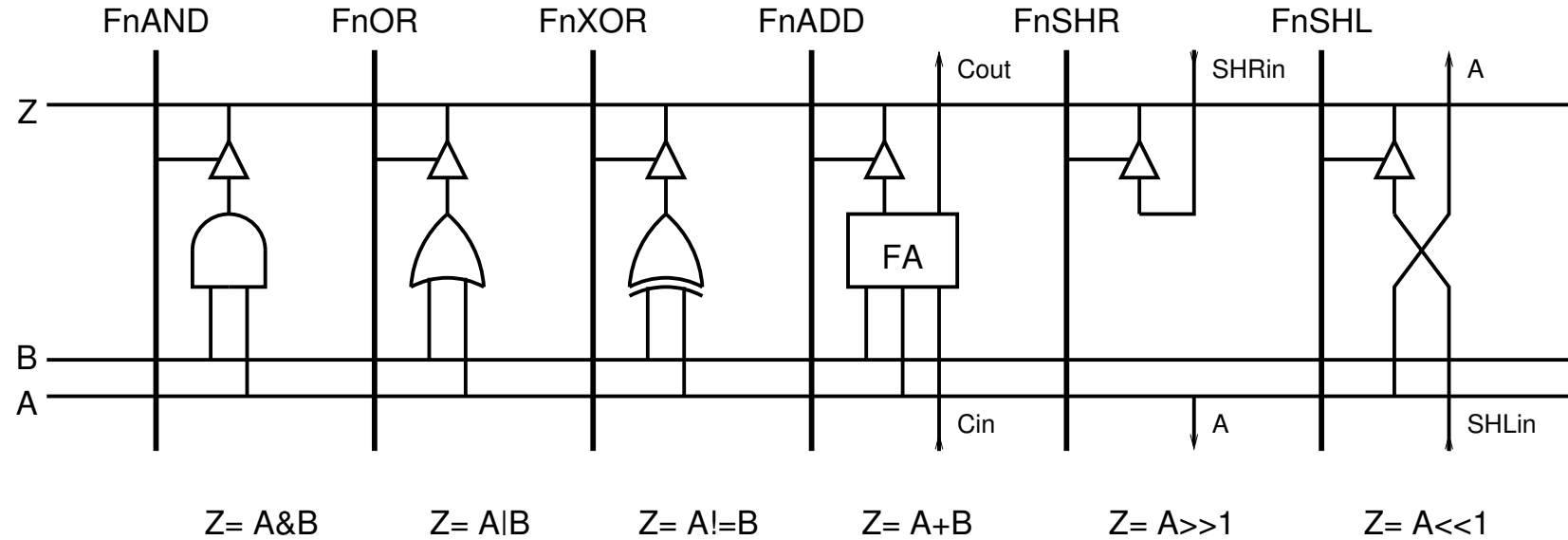

- Simple 1-bit ALU.
- The control lines select which function of A and B is fed to Z.
- Some functions, e.g. Add, require extra data I/O.


Bit Slicing

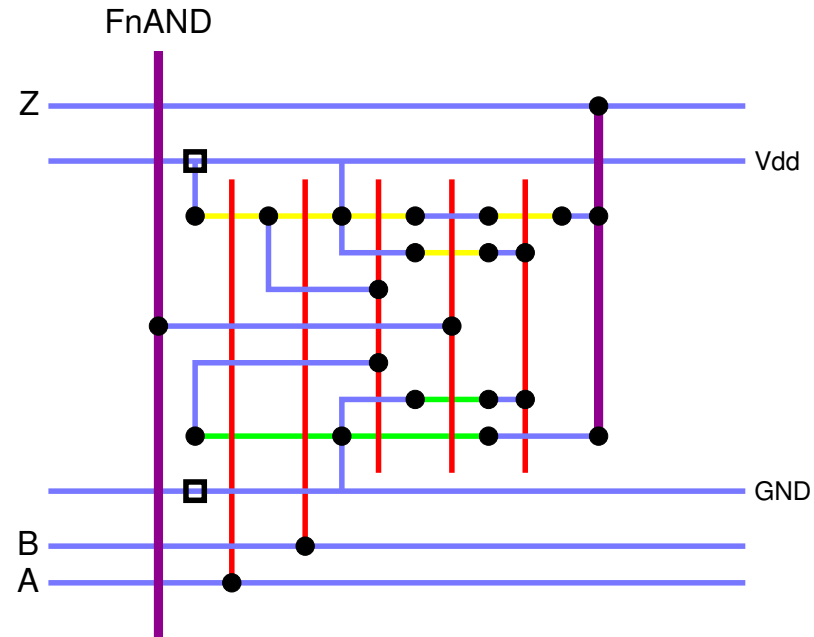 

- Data busses horizontal, control lines vertical.
- Compact gate matrix implementation¹.


¹bit slice designs can also be built around standard cells although the full custom approach used here gives better results

- Bit Sliced ALU (3-bits, scalable).

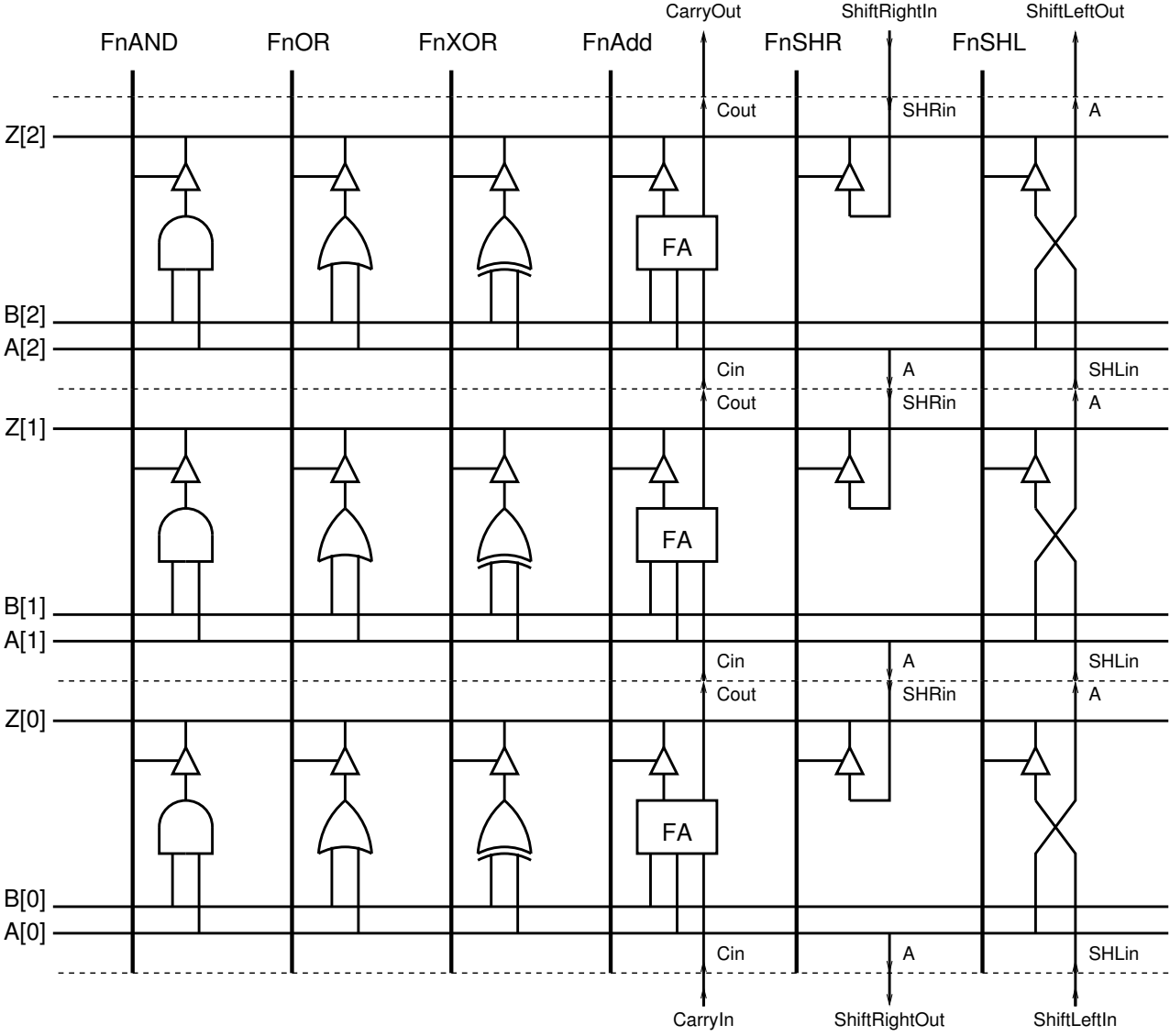


Bit Slicing

 
We can extend this principle to the whole *datapath*.



- 1-bit datapath.

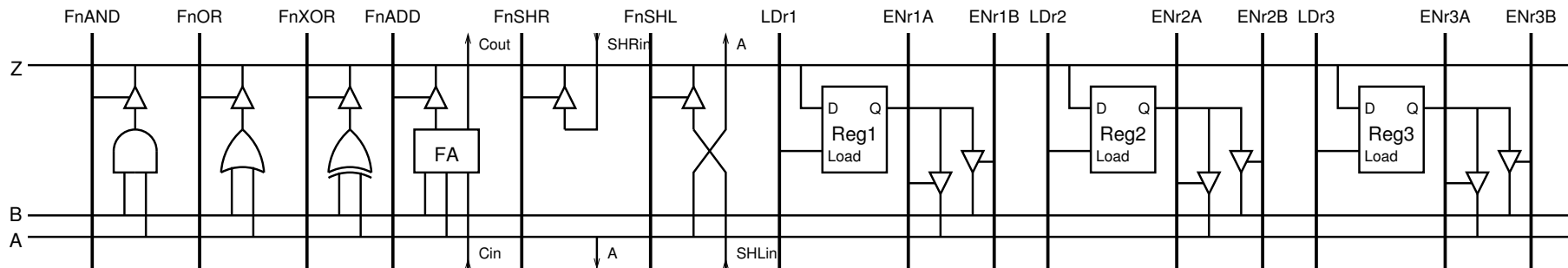


• Bit Sliced Datapath

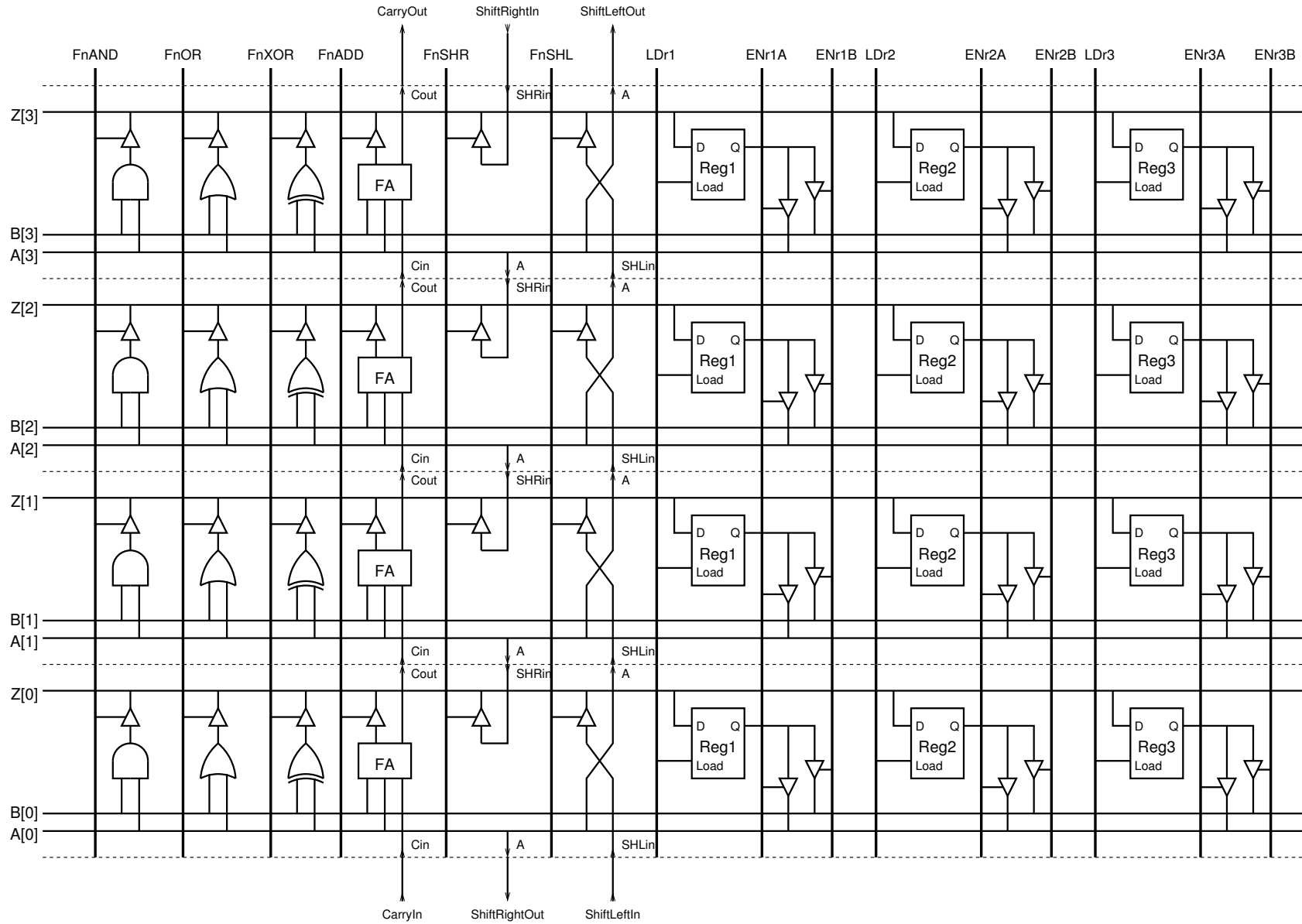


Bit Slicing


- Distributed Multiplexing

 

- Local Multiplexing

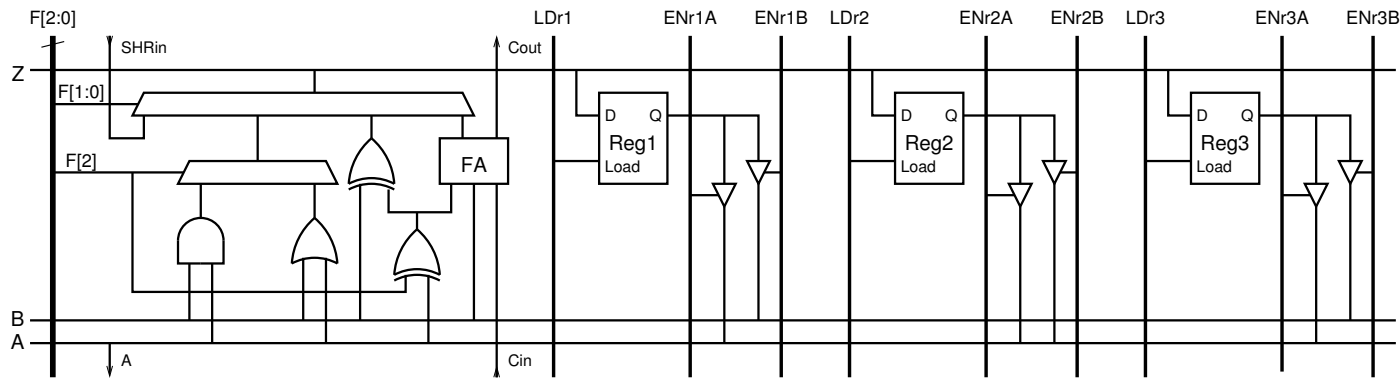


Bit Slicing - Example

 


Bit Slicing - Example

 
1 Bit ALU (no consideration of bitslicing)



Bitslice Design for ALU

 


Bit Slicing - Example

 

4011


Bit Slicing

 

4012


Bit Slicing

Original Bitslice Design for ALU

 


Modified Bitslice Design for ALU

 - Wiring is arranged so that no over cell routing is required.



Bit Slicing

Single Bit Shift

 


This simple ALU bitslice now supports 4 functions

- $Y = A + B$
- $Y = A | B$
- $Y = (A \gg 1) + B$
- $Y = (A \gg 1) | B$

Bit Slicing


Multi-Bit Shift

 This barrel shifter bitslice includes wiring for 4 bit right shift, wiring for 2 bit right shift and wiring for 1 bit right shift.



- $Y = A \gg \text{RShift}[2:0]$


Bit Slicing

 


Bit Slicing

Multi-Bit Rotate

 
By providing extra feedthrough paths we can create a bitslice for multi-bit rotation.



 N.B. Most single bit rotate functions will *rotate through the carry*. This barrel rotation, based on the SPARC implementation, does not make use of the carry for input or output.




Bit Slicing

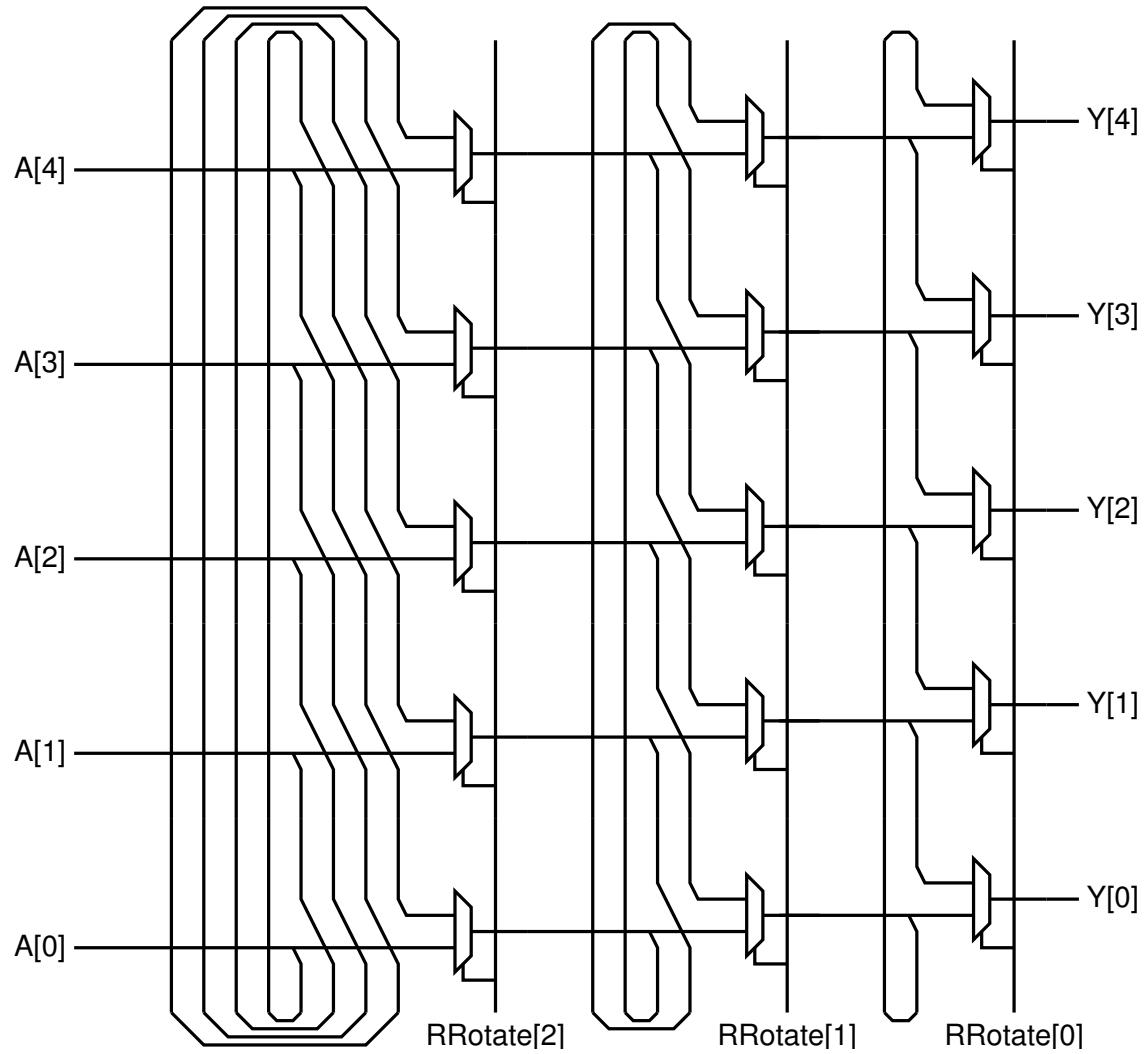

4020

Bit Slicing

1 bit ALU	4 bit Carry Lookahead Unit	Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3
1 bit ALU	4 bit Carry Lookahead Unit	Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3
1 bit ALU	4 bit Carry Lookahead Unit	Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3
1 bit ALU		Reg1	Reg2	Reg3

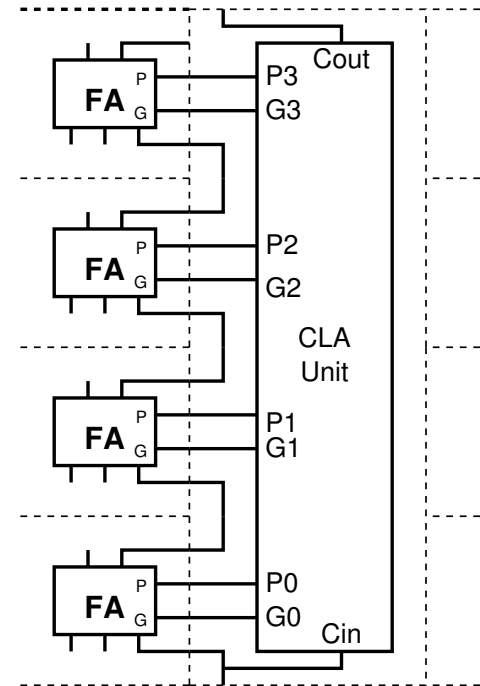

- Bitslice Exceptions

Where full bitslicing is not suitable we attempt to disrupt the bitslice as little as possible.